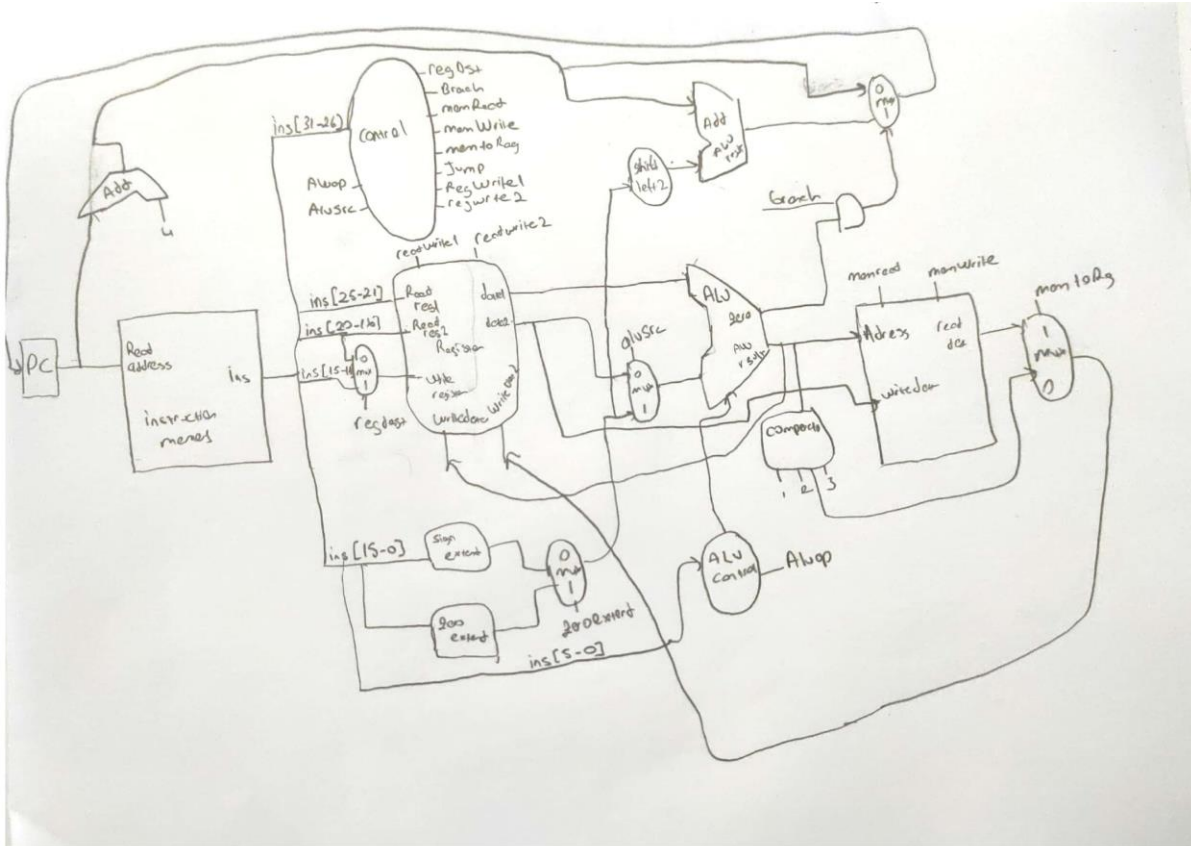


CSE 331/503
COMPUTER ORGANIZATION FALL 2020
HOMEWORK 4 REPORT

OZAN GEÇKİN 1801042103

Single Cycle Datapath Design:




CamScanner ile tarandı

I used following schema. I designed all the modules I use in my datapath.

Modules

Instruction Memory:

 I use it to hold my instructions. It receives 32 bit address and clock as input. It gives 32 bit instruction as output.




Instruction Memory Test:

```
sim:/instruction_testbench/PC
VSIM 6> step -current
# Inst [ 1]-- Opcode=000000 [00], Rs=01000 [08], Rt=00011 [03], Imm=0000100010100000 [08a0]
# Inst [ 2]-- Opcode=001010 [0a], Rs=11111 [1f], Rt=00101 [05], Imm=0000010011111111 [04ff]
# Inst [ 3]-- Opcode=000100 [04], Rs=00001 [01], Rt=00101 [05], Imm=0000000000000011 [0003]
# Inst [ 4]-- Opcode=000000 [00], Rs=01000 [08], Rt=01001 [09], Imm=1111100010100001 [f8a1]
# Inst [ 5]-- Opcode=000000 [00], Rs=01000 [08], Rt=01001 [09], Imm=1111100010100101 [f8a5]
# Inst [ 6]-- Opcode=000000 [00], Rs=01000 [08], Rt=01001 [09], Imm=1111100010000000 [f880]
# Inst [ 7]-- Opcode=100011 [23], Rs=01001 [09], Rt=01000 [08], Imm=0000000000001111 [000f]
# Inst [ 8]-- Opcode=000000 [00], Rs=01010 [0a], Rt=01110 [0e], Imm=0111100010000010 [7882]
# Inst [ 9]-- Opcode=000000 [00], Rs=11111 [1f], Rt=10000 [10], Imm=1000100000100010 [8822]
# Inst [10]-- Opcode=000000 [00], Rs=11110 [1e], Rt=10001 [11], Imm=1001000000100011 [9023]
# Inst [11]-- Opcode=000000 [00], Rs=10010 [12], Rt=11101 [1d], Imm=1010000000101010 [a02a]
# Inst [12]-- Opcode=000000 [00], Rs=10110 [16], Rt=10101 [15], Imm=1010100000101011 [a82b]
# Inst [13]-- Opcode=001000 [08], Rs=10101 [15], Rt=10111 [17], Imm=0000000000010010 [0012]
# Inst [14]-- Opcode=001100 [0c], Rs=10111 [17], Rt=11001 [19], Imm=0000000000011011 [001b]
# Inst [15]-- Opcode=001001 [09], Rs=11001 [19], Rt=11010 [1a], Imm=0000000000100011 [0023]
# Inst [16]-- Opcode=001101 [0d], Rs=11010 [1a], Rt=11011 [1b], Imm=0000000000011001 [0019]
# Inst [17]-- Opcode=001010 [0a], Rs=11101 [1d], Rt=11100 [1c], Imm=0000000000011101 [001d]
# Inst [18]-- Opcode=100011 [23], Rs=11110 [1e], Rt=11111 [1f], Imm=0000000001000000 [0040]
# Inst [19]-- Opcode=110000 [30], Rs=11111 [1f], Rt=11110 [1e], Imm=0000000010000000 [0080]
# Inst [20]-- Opcode=001111 [0f], Rs=01011 [0b], Rt=11101 [1d], Imm=0000000001111111 [007f]
# Inst [21]-- Opcode=000100 [04], Rs=00011 [03], Rt=00111 [07], Imm=0000000000010110 [0016]
# ** Note: $finish : C:/altera/13.1/workspace/hw/instruction_testbench.v(13)
# Time: 420 ns Iteration: 0 Instance: /instruction_testbench
```

Register Modul:

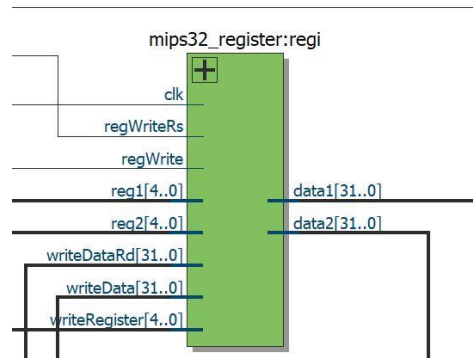You redesigned it according to the New R-type instructions. There were 2 data entries. You can see all inputs and outputs in RTL view.



Register Modül Test:


Register Before:

Test Code:

Register After:

[illegible]

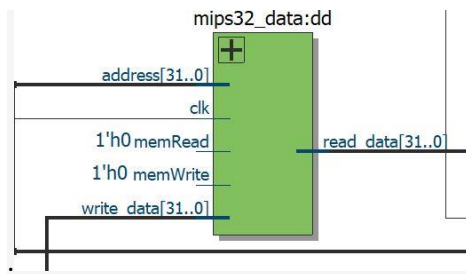I use it to write and read data. You can see all inputs and outputs in RTL view.



Data Memory Test:

Data Before:

Data After:

[illegible]



Test Code:

```
sim:/mips32_data_testbench/memRead \
sim:/mips32_data_testbench/clock
V$IM 5> step -current
# Memory store edilen data: 11111111111111111111111111111111
# signal_mem_write=1, signal_mem_read=1, clk=1, write_data=11111111111111111111111111111111, address=00000000000000000000000000000000, read_data=11111111111111111111111111111111
V$IM 6>
```

Control Unit:

I have generated my signals using the Truth table. The control unit takes opcode as input. And it generates the signals required for the instruction to occur.

	RegDst	ALUSrc	MemToReg	RegWrite	MemRead	MemWrite	Branch	ALUOp2	ALUOp1	ALUOp0	Jump	RegWrite
R-Type	1	0 0	0	1	0	0	0	0	1	0	0	1
J	X	X X	X	0	0	0	0	X	X	X	1	0
ori	0	1 0	0	1	0	0	0	1	0	0	0	0
lw	0	0 1	1	1	1	0	0	0	0	0	0	0
sw	X	0 1	X	0	0	1	0	0	0	0	0	0
beq	X	0 0	X	0	0	0	1	0	0	0	0	0

 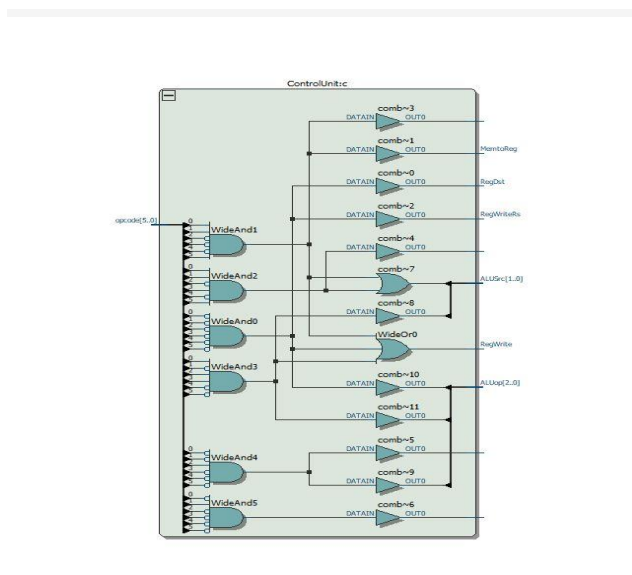

Control Unit Test:


```

sim:/ControlUnit_testbench/branch \
sim:/ControlUnit_testbench/RegWrite
VSIM 5> step -current
# opcode=100011, regDst=0,ALUSrc=01,regWire=1,memRead=1,MemToReg=0,memWrite=1,brach=0,aluop=000,jump=0,RegWriteRs=0
# opcode=101011, regDst=0,ALUSrc=01,regWire=0,memRead=0,MemToReg=1,memWrite=0,brach=0,aluop=000,jump=0,RegWriteRs=0
# opcode=000000, regDst=1,ALUSrc=00,regWire=1,memRead=0,MemToReg=0,memWrite=0,brach=0,aluop=010,jump=0,RegWriteRs=1
VSIM 6>

```

ALU Control Unit:

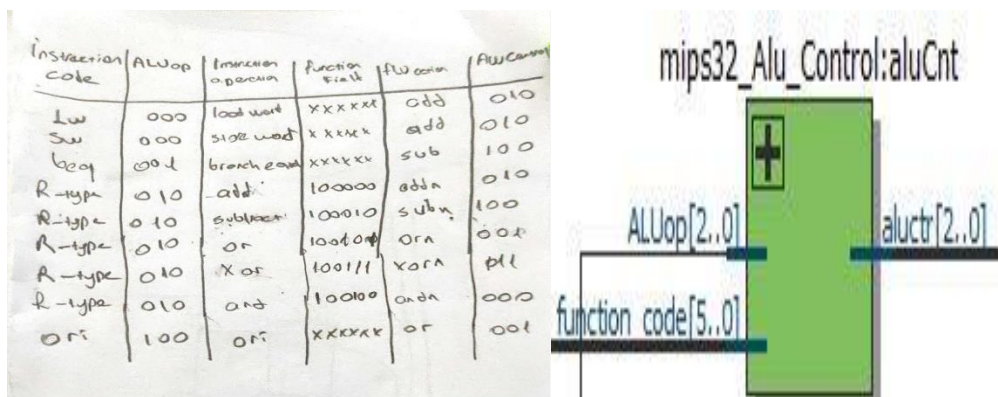It generates the signal to choose which action the ALU does. It receives the function code and the aluop. It receives the ALU from the control unit.



ALU Control Test:


```

VSIM 5> step -current
# aluOp=010,func=100000,aluctr=010
# aluOp=000,func=100000,aluctr=010
# aluOp=001,func=001111,aluctr=100
VSIM 6>

```

ALU Module:

 ALU performs operations according to the signal coming from the control and draws results.




ALU Module Test:

```
sim:/alu32_bit_testbench/sel \
sim:/alu32_bit_testbench/R
VSIM 5> step -current
# A=00000000000000000000000000000001 ,B=00000000000000000000000000000001 ,sel=000, R=00000000000000000000000000000001
# A=00000000000000000000000000000001 ,B=00000000000000000000000000000001 ,sel=001, R=00000000000000000000000000000101
# A=00000000000000000000000000000001 ,B=00000000000000000000000000000001 ,sel=010, R=00000000000000000000000000000110
# A=00000000000000000000000000000001 ,B=00000000000000000000000000000001 ,sel=011, R=00000000000000000000000000000100
# A=00000000000000000000000000000001 ,B=00000000000000000000000000000001 ,sel=100, R=00000000000000000000000000000100
VSIM 6>
```

Comparator Module:

 Comparator produces the value by comparing the content of Rs and Rd with 0 according to the result from alu.




Comparator Module Test:

```
sim:/mips32_Comparator_testbench/rd
VSIM 5> step -current
# A=000000000000000000000000000001010,rd=00000000000000000000000000000010
# A=111111111111111111111111111111101,rd=00000000000000000000000000000011
# A=000000000000000000000000000000000,rd=00000000000000000000000000000001
VSIM 6>
```


Mux 2 to 1 Module:

 It selects one of the 2 inputs according to the incoming signal.




Mux 2 to 1 Module test:

```
VSIM / mux2to1_32bit_testbench/ sel
VSIM 6> step -current
# c0=00000000000000000000000000000000 c1=00000000000000000000000000000011 sel=0 out=00000000000000000000000000000000
# c0=00000000000000000000000000000000 c1=00000000000000000000000000000011 sel=1 out=00000000000000000000000000000011
VSIM 7>
```

Mux 4 to 1 Module:

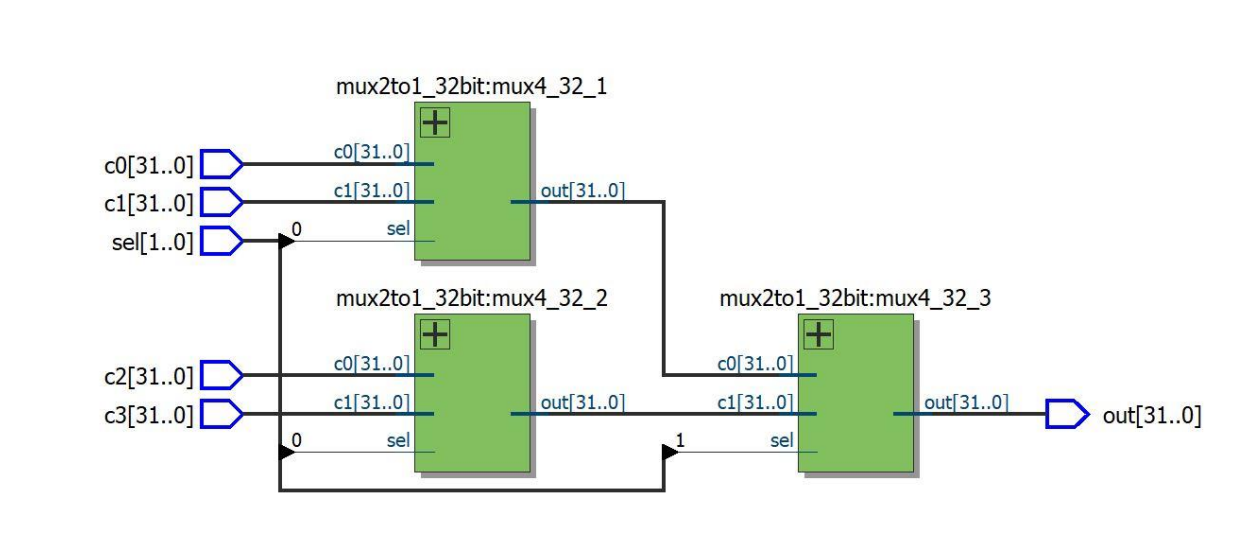It selects one of the 4 inputs according to the incoming signal. I used Mux 2 to 1 in its production.




Mux 4 to 1 Module Test:

```
SIM 5> step -current
| c0=00000000000000000000000000000000 c1=00000000000000000000000000000001 c2=00000000000000000000000000000010 c3=00000000000000000000000000000011 sel=00 out=00000000000000000000000000000000
| c0=00000000000000000000000000000000 c1=00000000000000000000000000000001 c2=00000000000000000000000000000010 c3=00000000000000000000000000000011 sel=01 out=00000000000000000000000000000001
| c0=00000000000000000000000000000000 c1=00000000000000000000000000000001 c2=00000000000000000000000000000010 c3=00000000000000000000000000000011 sel=10 out=00000000000000000000000000000010
| c0=00000000000000000000000000000000 c1=00000000000000000000000000000001 c2=00000000000000000000000000000010 c3=00000000000000000000000000000011 sel=11 out=00000000000000000000000000000011
SIM 6>
```

Mux 8 to 1 Module :

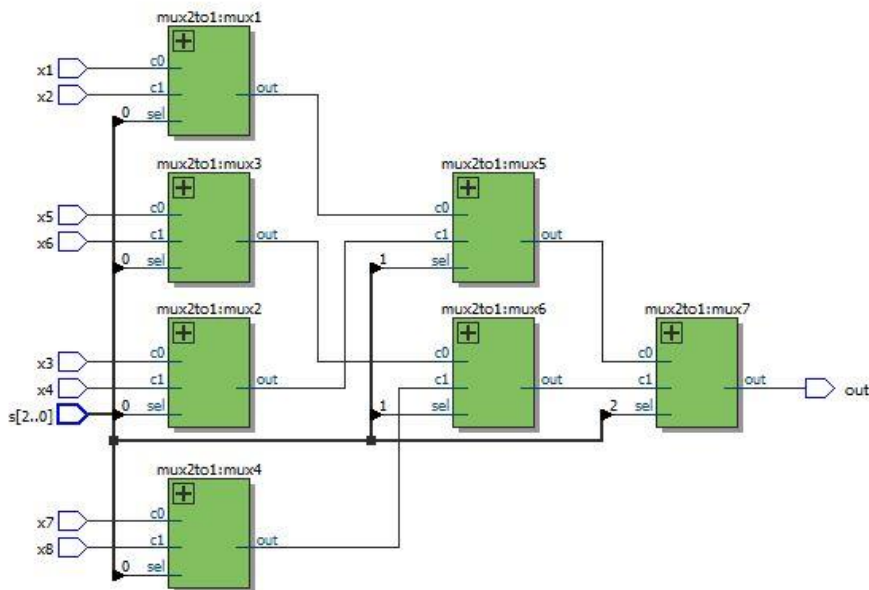It selects one of the 8 inputs according to the incoming signal. I used Mux 2 to 1 in its production.




Mux 8 to 1 Module Test:

```
SIM 5> step -current
| c1=00000000000000000000000000000000 c2=00000000000000000000000000000001 c3=00000000000000000000000000000010 c4=00000000000000000000000000000011 c5=00000000000000000000000000000001 c6=00000000000000000000000000000000 c7=00000000000000000000000000000000 c8=00000000000000000000000000000000
| sel=000 out=00000000000000000000000000000000
```

Adder Module :

Adds 2 32-bit numbers.

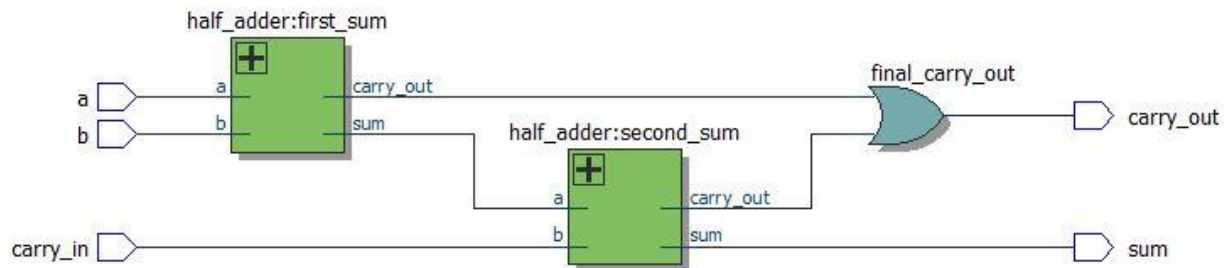


Adder Module Test:

[illegible]

Subtract Module:

Subs 2 32-bit numbers.

 

Subtract Test Module

[illegible]


And Module:

Ands 2 32-bit numbers.

And Module Test:

SignExtend Module:

 According to Most Significant bit, it completes the number from 16 bits to 32 bits.



SignExtend Module Test:

```
sim:/signExtend_testbench/out
VSIM 5> step -current
# inp=0000001111111111,out=00000000000000000000001111111111
```

ZeroExtend Module:

It completes a 16-bit number with a leading 0 to 32 bits.

ZeroExtend Module Test:

```
sim:/zeroExtend_testbench/A
VSIM 5> step -current
# A=0101010101000000,ZeroExtend=000000000000000001010101000000
```

Program Counter :

I designed it for the jump and branch instructions. He gets instruction, jump signal, branch signal, clock. And holding the counter returns the omitted instruction.

NOT: I ran all my modules separately, but I had problems integrating with the datapath. I have shown that all my modules are working by adding their tests to my report. Thank you very much for your understanding and teaching in the whole semester.